

# Balanced Y- Connected Voltage Source

✓ Line currents equal phase Currents


$$I_L = I$$

✓ Phase voltages are

$(V_{an}, V_{bn}, V_{cn})$

✓ Line voltages are

$(V_{ab}, V_{bc}, V_{ca})$

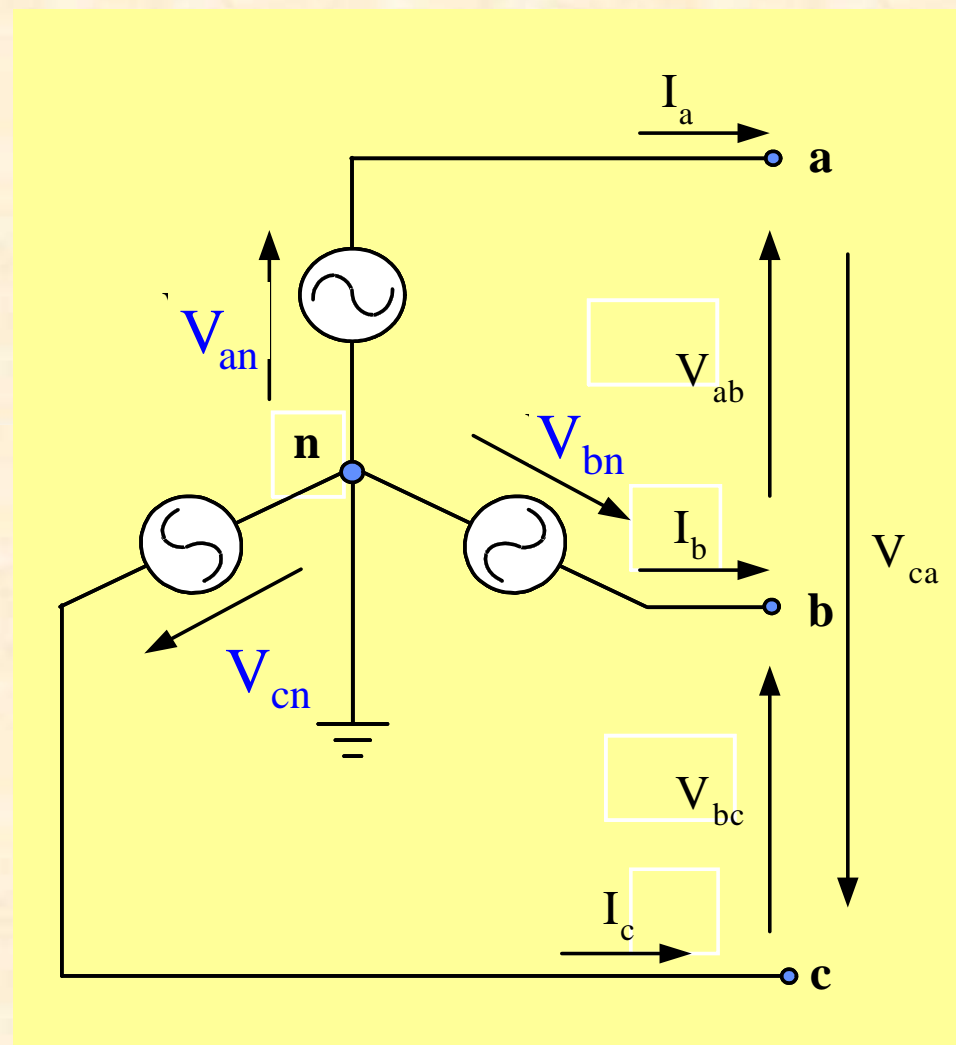

# Phase Diagram of Line and Phase Voltages (+ve Sequence)

## □ PHASE VOLTAGE

$$V_{an} = V \angle 0^\circ$$

$$V_{bn} = V \angle -120^\circ$$


$$V_{cn} = V \angle +120^\circ$$

## □ LINE VOLTAGE

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{bc} = V_{bn} - V_{cn}$$

$$V_{ca} = V_{cn} - V_{an}$$

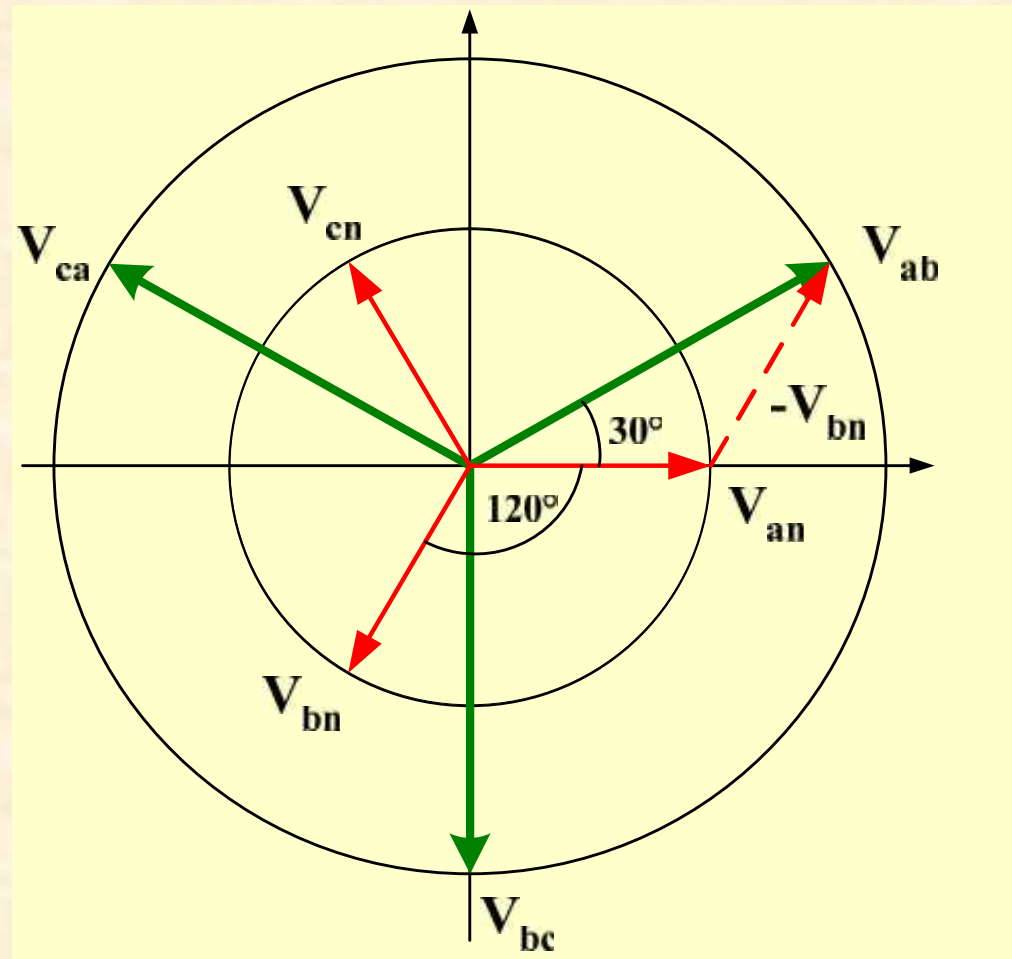

# Relation Between Line and Phase Voltages (+ve Sequence)

**LINE  
VOLTAGE  
( $V_L$ )**



$$V_{ab} = \sqrt{3} V \angle 30^\circ$$

$$V_{bc} = \sqrt{3} V \angle -90^\circ$$

$$V_{ca} = \sqrt{3} V \angle 150^\circ$$



$$|V_L| = \sqrt{3} |V_w|$$

$$\angle V_L = \angle V_w + 30^\circ$$



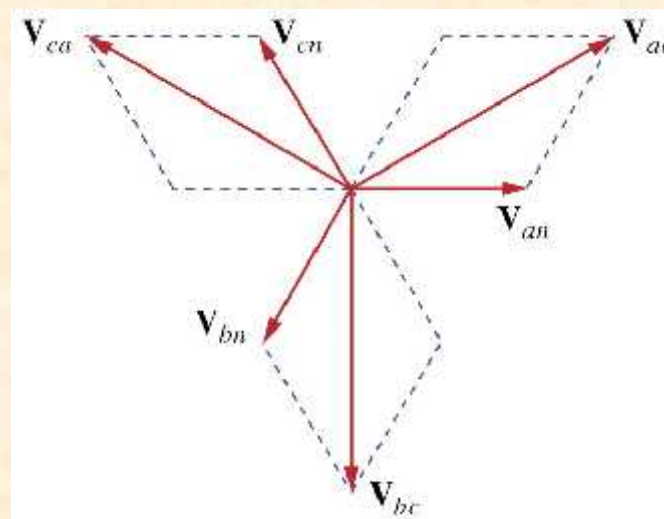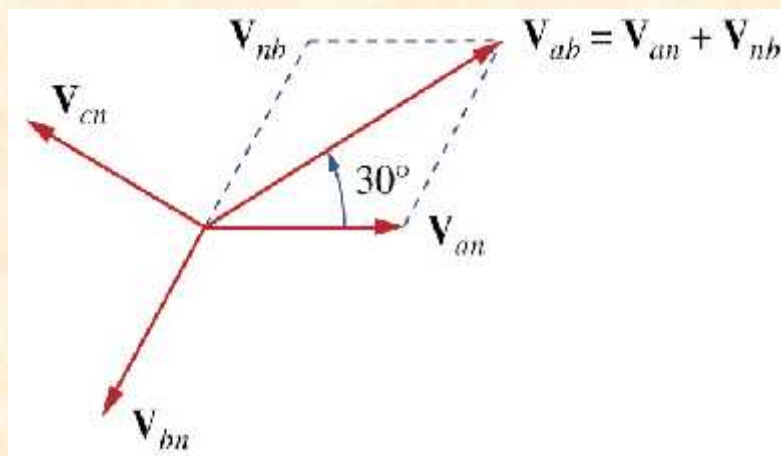
# Conclusions for Balanced Y-connected Voltage Source


- **Balanced line voltages** are equal in magnitude and are out of phase with one another by **120** degrees
- Line voltages sum up to zero ( $V_{ab} + V_{bc} + V_{ca} = 0$ )
- The magnitude of line voltages is  $\sqrt{3}$  times the magnitude of the phase voltages
- Line Voltages **lead** their corresponding phase voltages by 30 degrees (for +ve sequence)



# Balanced Y-connected Load

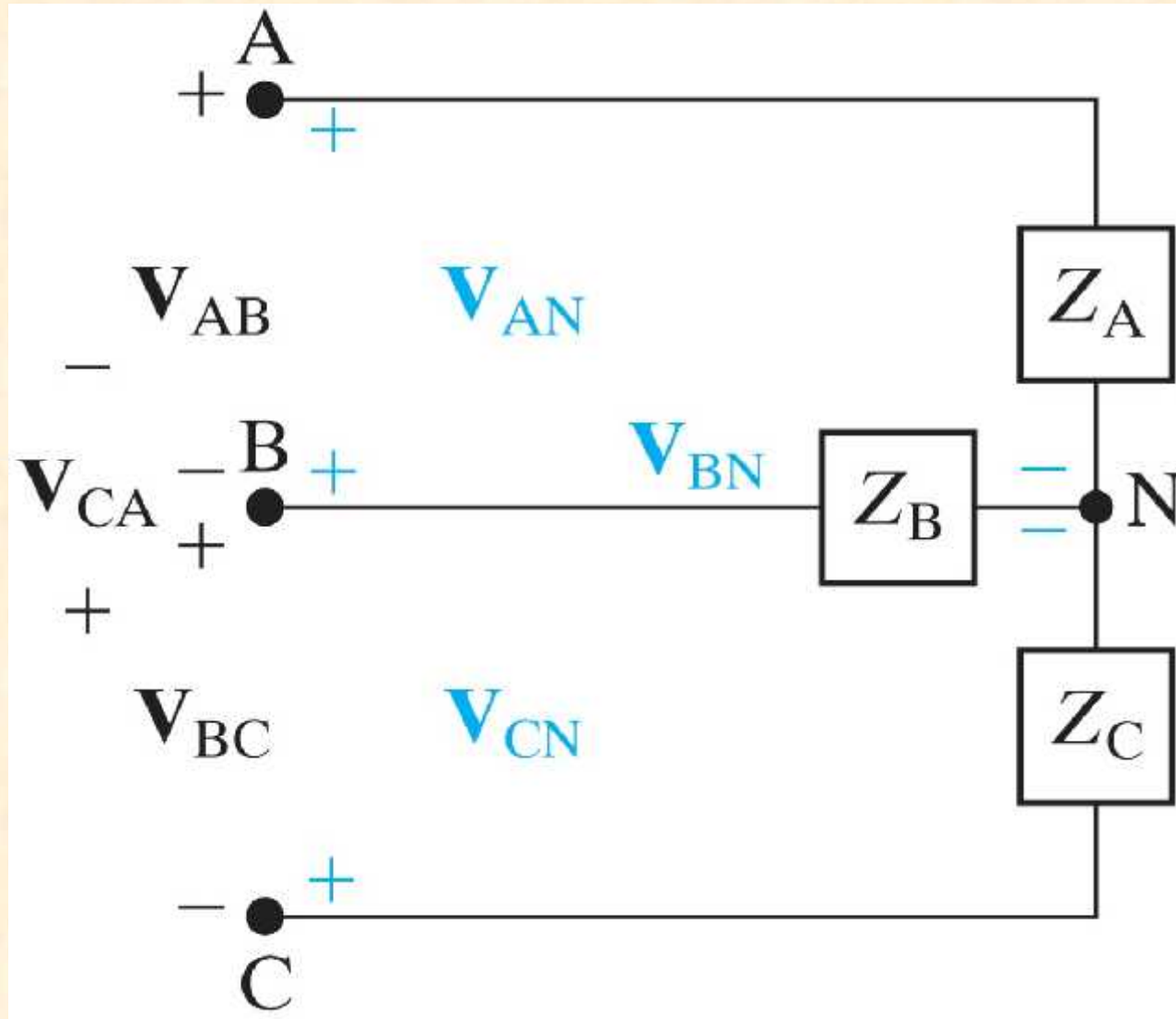

# Balanced Y-connected Load

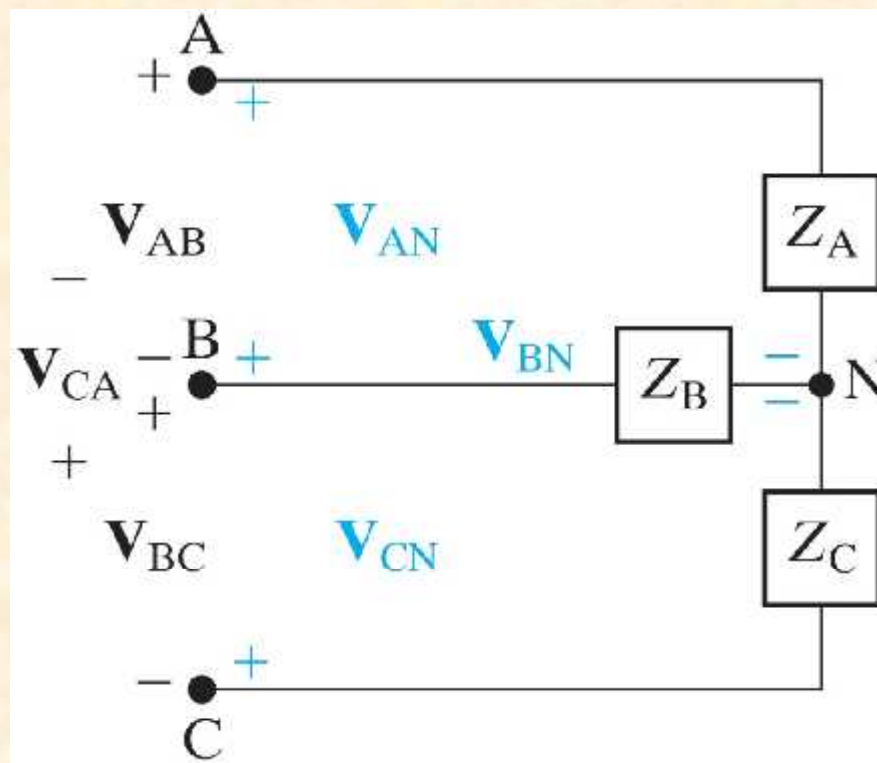

$$V_{AB} = V_{AN} - V_{BN}$$

**Line Voltages**

$$V_{BC} = V_{BN} - V_{CN}$$


**Phase Voltages**

$$V_{CA} = V_{CN} - V_{AN}$$




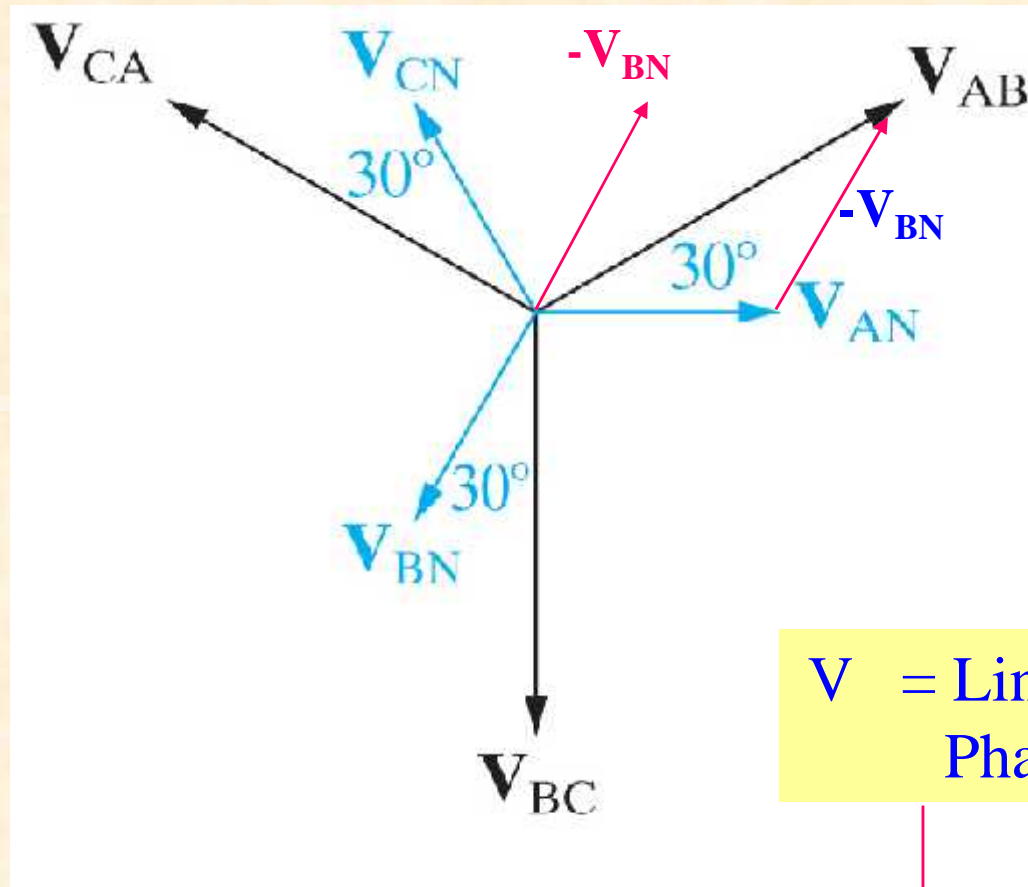
# Line and Phase Voltages for Balanced Y-connected Load



$V$  = Line-to-Neutral, or  
Phase Voltage

$$V_{AB} = V_{AN} - V_{BN} = \sqrt{3} V$$




# Conclusions for Balanced Y-Connected System

- The Line currents **equal** phase Currents
- The amplitude of the line-to-line voltage is equal to  $\sqrt{3}$  times the amplitude of the phase voltage
- The line-to-line voltages form a balanced set of 3-phase voltages
- The set of line-to-line voltages **leads** the set of line-to-neutral (phase) voltages by  $30^\circ$  (for +ve sequence)
- The set of line-to-line voltages **lags** the set of line-to-neutral (phase) voltages by  $30^\circ$  (for -ve sequence)





# Y-Y Three-Phase System (Four Wire)

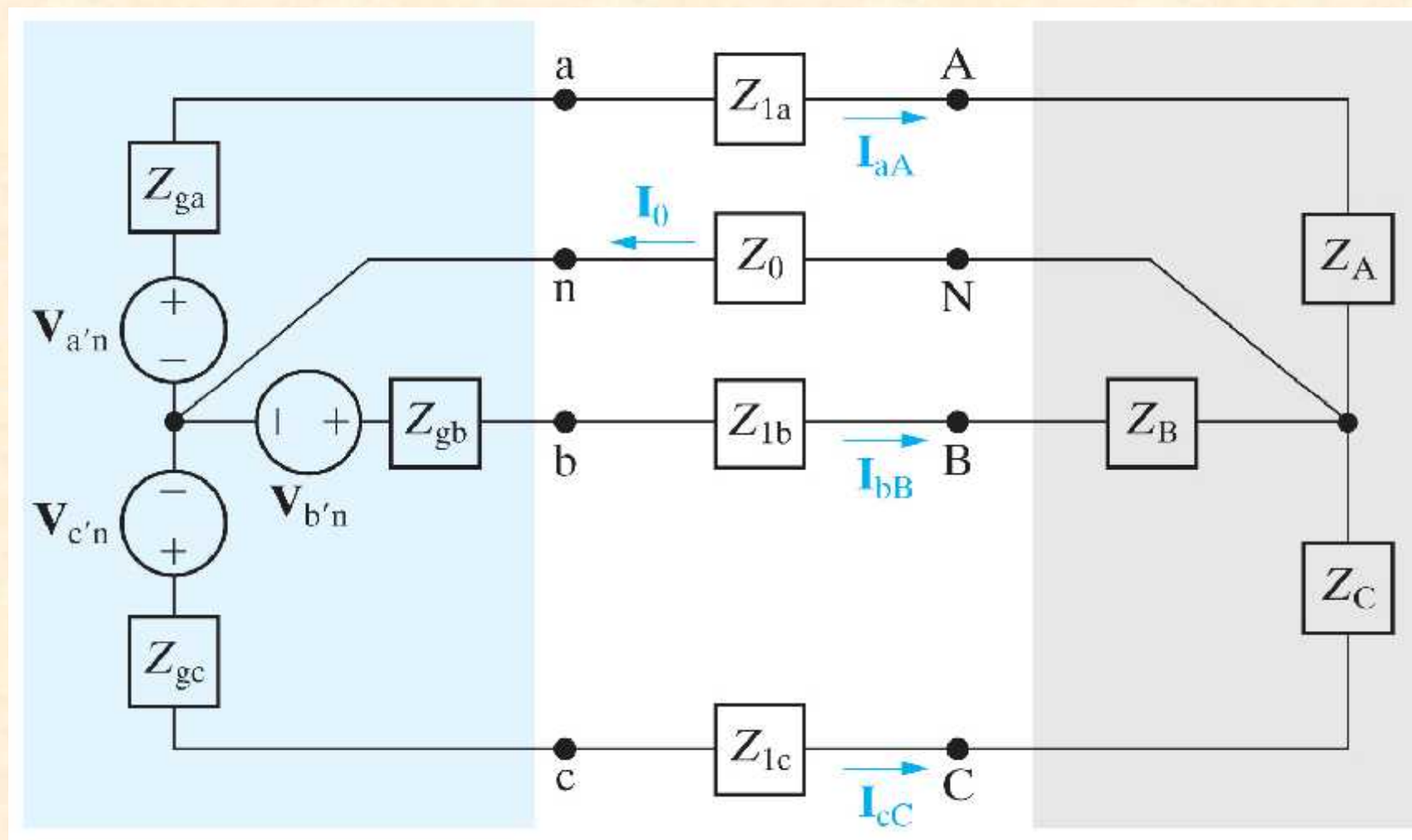

# Y-Y Three-Phase System (Four Wire)

- $Z_g$  represents the internal generator impedance per phase
- $Z_l$  represents the impedance of the line connecting the generator to the load
- $Z_{A,B,C}$  represents the load impedance per phase
- $Z_o$  represents the impedance of the neutral conductor



# Neutral Voltage for Y-Y System

➤ Using source neutral as a reference, the Node-Voltage equation at node N can be written as:

$$\frac{\mathbf{V}_N}{Z_o} + \frac{\mathbf{V}_N - \mathbf{V}_{a'n}}{Z_A + Z_{la} + Z_{ga}} + \frac{\mathbf{V}_N - \mathbf{V}_{b'n}}{Z_B + Z_{lb} + Z_{gb}} + \frac{\mathbf{V}_N - \mathbf{V}_{c'n}}{Z_C + Z_{lc} + Z_{gc}} = 0.$$

➤ *For a balance three-phase system;*

✓ Three-phase voltages are balanced,

✓  $Z_{ga} = Z_{gb} = Z_{gc}$  ,  $Z_{la} = Z_{lb} = Z_{lc}$  and  $Z_A = Z_B = Z_C$

$$Z_{\phi} = Z_A + Z_{la} + Z_{ga}$$



# Neutral Voltage for Y-Y System

➤ The neutral voltage can be given by:

$$\mathbf{V}_N \left( \frac{1}{Z_\psi} + \frac{3}{Z_\phi} \right) = \frac{\mathbf{V}_{a'n} + \mathbf{V}_{b'n} + \mathbf{V}_{c'n}}{Z_\phi}.$$

□ As the three-phase voltages are balanced (i.e.  $\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$ ), therefore the neutral voltage must be equal zero

$$\mathbf{V}_N = 0.$$

